

ALTERNATING CURRENT

Challenging **MCQ** questions by The Physics Cafe

Compiled and selected by The Physics Cafe



- 1 (a) Fig. 5.1 below shows an alternating voltage supply given by $V = V_0 \cos\left(\frac{2\pi}{T}t\right)$ connected to four diodes numbered 1, 2, 3 and 4 and a resistor R .


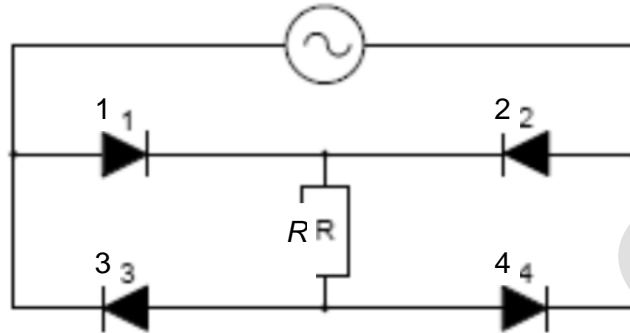


Fig 5.1

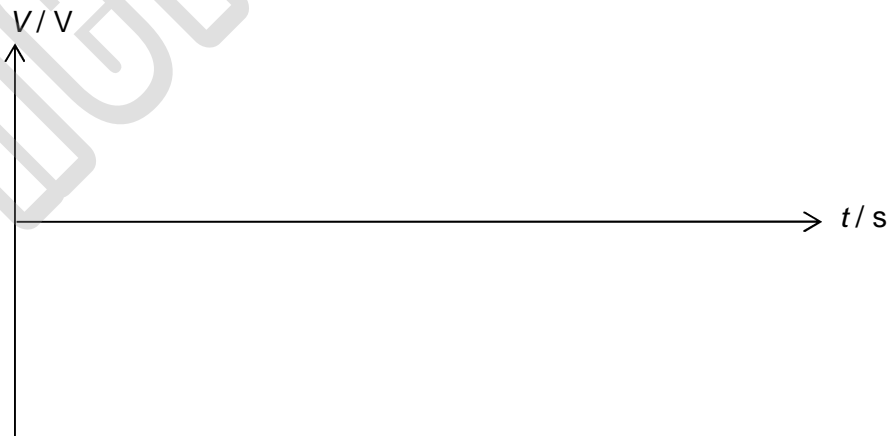- (i) On the axes given below, sketch and label the voltage-time graph of the resistor for at least two cycles when all four diodes are in use. Clearly label the period of each cycle. [2]



- (ii) If diode 4 is removed, leaving a break in the circuit, sketch and label the new voltage-time graph of the resistor for at least two cycles. [2]



(b) A power station produces **20.0 MW** of power for delivery to a town some distance away. This power is generated at **32.0 kV** and then stepped up to **240 kV** using an ideal transformer before transmission. The total resistance of the transmission cables is **5.0 Ω** .


(i) State the turns ratio of the secondary coil to the primary coil in this transformer.

turns ratio = [1]

(ii) Explain why it is more economical to step up to **240 kV** before transmitting electrical power to the town. Justify your answer in terms of power loss in the transmission cables.

.....
.....
..... [3]

Ans (a) (i)

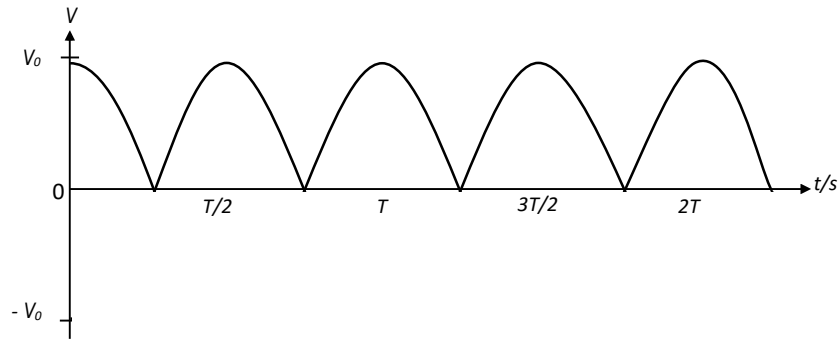

[M1] for correct shape


$V = 0$ when $t = 0$

sharp edges at $T/4$

at least 2 cycles should be drawn

[A1] for correct label of V_0 and T

(ii)

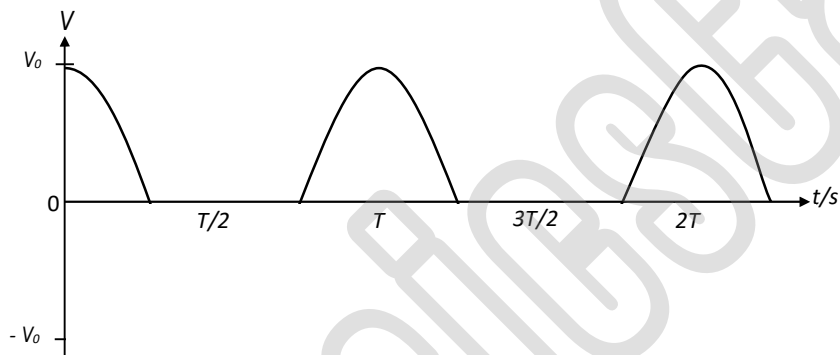

[M1] for correct shape (ecf is given if student show understanding that only half of the cycle exists and the graph can only be in either the positive or negative axis).

[A1] for correct label of V_0 and T

(b) (i) Turns ratio $\frac{N_s}{N_p} = \frac{240}{32} = 15:2$

[A1]

(ii) Since power in the primary coil = power in secondary coil

At 240 kV,

$$P_{in} = P_{out} = 20 \times 10^6 \text{ W}$$

$$I_{out} \times V_{out} = 20 \times 10^6 \text{ W}$$

$$I_{out} = \frac{20 \times 10^6}{240 \times 10^3} = 83.3 \text{ A}$$

$$P_{cables} = I^2 R = 83.3^2 \times 5.0 = 34.7 \text{ kW}$$

[M1]

At 32.0 kV,

$$I_{out} = \frac{20 \times 10^6}{32.0 \times 10^3} = 625 \text{ A}$$

$$P_{loss} = I^2 R = 625^2 \times 5.0 = 1.95 \text{ MW}$$

[M1]

Since less power is lost transmitting at 240 kV, it is more economical to transmit at 240 kV.

[A1]

2

- (a) An electric kettle, designed for travellers, can be used with different voltages. It is rated **700 W** for a **240 V** alternating supply. Determine its power output when used on a **120 V** direct supply.

[1]

- (b) A simple transformer connected with a circuit is illustrated in **Fig. 5.1**

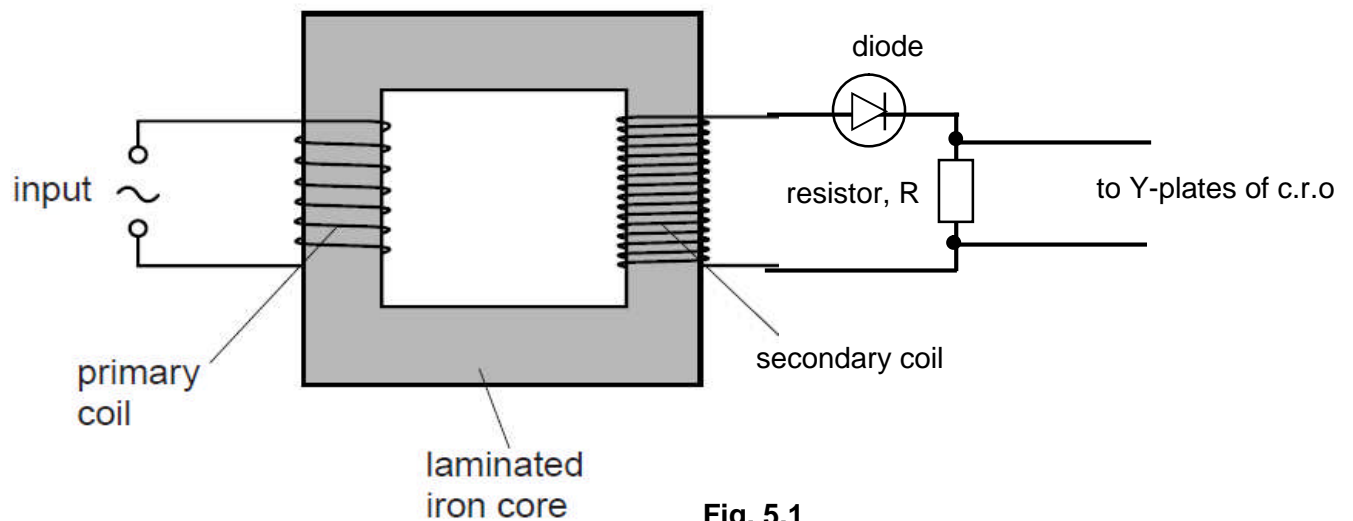


Fig. 5.1

- (i) An ideal transformer has **300 turns** on the primary coil and **8100 turns** on the secondary coil. The root-mean-square input voltage to the primary coil is **9.0 V** of frequency **50 Hz**. Calculate the peak voltage in the secondary coil.

[1]

- (ii) A cathode-ray oscilloscope (c.r.o) Y-plates connected across the load resistor R and the trace in **Fig. 5.2** is seen. Calculate the Y-plate sensitivity of the c.r.o.

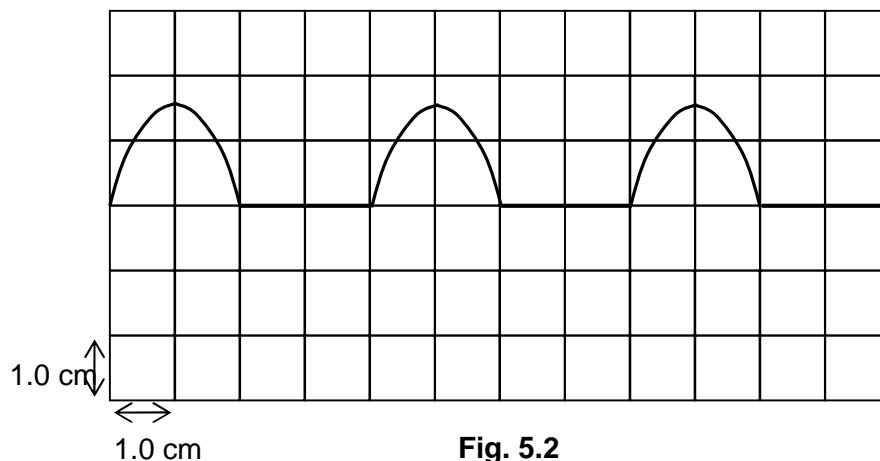


Fig. 5.2

[2]

- (iii) The diode is now removed from the circuit in Fig. 5.1. On Fig. 5.3, sketch a graph which shows how the power of the load resistor, R, of resistance 5.0Ω varies with time. [3]

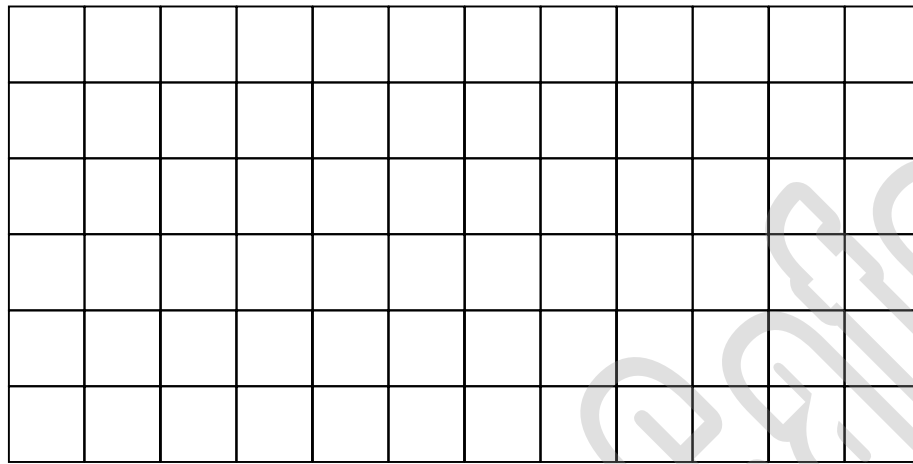


Fig. 5.3


- Ans a. Using Power, $P = V^2/R$
 $R = V^2/P = 240^2/700 = 82.3 \Omega$
 New power dissipated $P' = V'^2/R = 120^2/82.3 = 175 \text{ W}$
- bi. Using $N_p/N_s = V_p/V_s$
 $300/8100 = 9/V_s$
 $V_s = 243 \text{ V (rms)}$
 Peak voltage, $V_o = 243 \times \sqrt{2} = 343 \text{ V}$
- bii 1.5 cm represents 343 V
 1 cm represents 229 V
 Hence the sensitivity is 229 Vcm^{-1}

5biii

$$\text{Power} = V_o^2/R = 343^2/5.0$$

$$= 23.5 \text{ kW}$$

$$T = 1/f = 1/50 = 0.02 \text{ s}$$

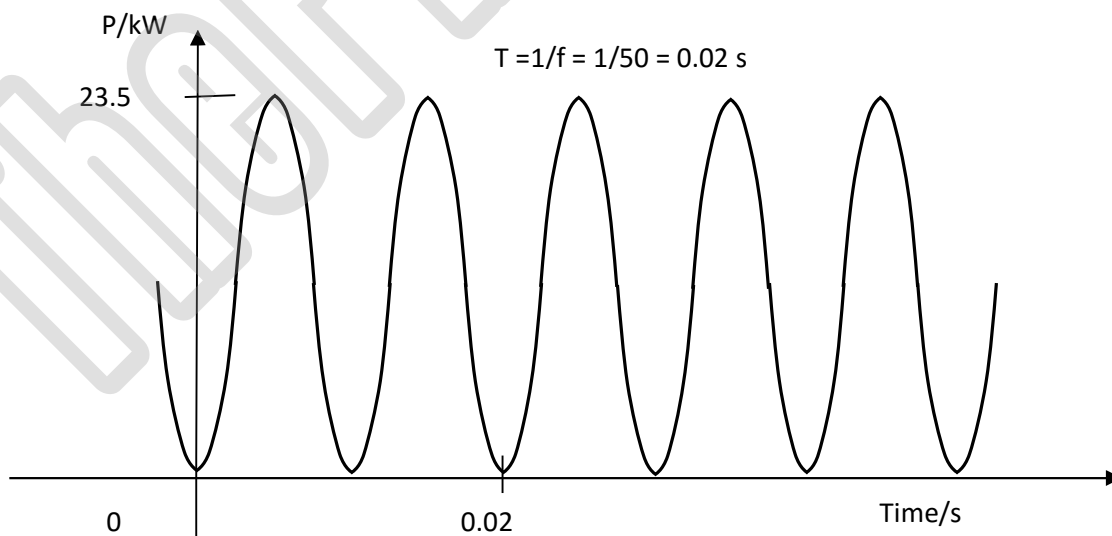

- 3 The primary coil of an ideal transformer has **100 turns** and is connected to a **15V** root-mean-square (r.m.s.) supply at **50 Hz**. The secondary coil has **1600 turns** and is connected to a resistor of resistance **120 Ω** as shown in Fig. 5.1

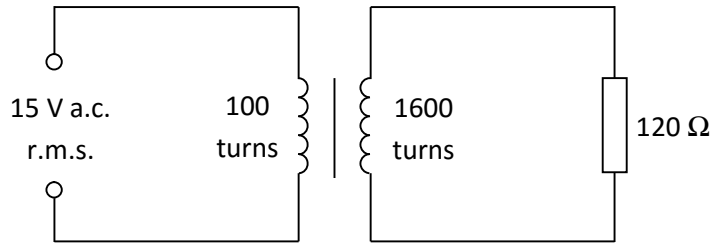


Fig. 5.1

- (a) Determine the r.m.s. value of the current in the resistor.

current = A [2]

- (b) The variation with time t of the current I in the resistor is given by $I = I_o \sin \omega t$.

On Fig. 5.2, sketch the variation with time t of the power P dissipated in the resistor from $t = 0$ to $t = 0.020$ s.



Fig. 5.2

[2]

(c) On Fig. 5.3, sketch the variation of the net amount of charge Q which flowed past a point in the resistor from $t=0$ to $t=0.020$ s. (Numerical values for the charge are not expected.)

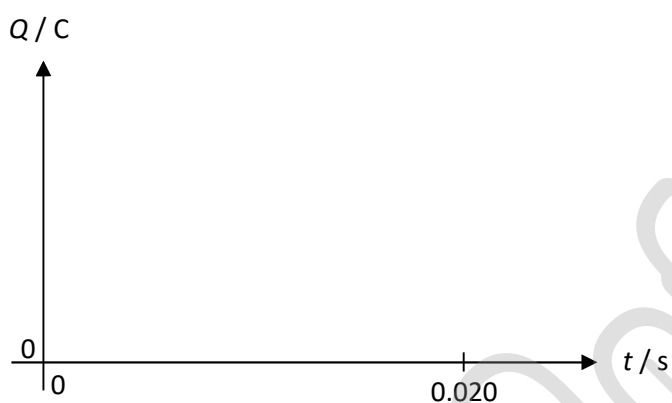


Fig. 5.3

[1]

Ans (a) $\frac{V_s}{V_p} = \frac{N_s}{N_p}$
 $\frac{V_s}{15} = \frac{1600}{100}$
 $V_s = 240 \text{ V}$

Since $R = \frac{V_s}{I_s}$,
 $I_s = \frac{240}{120} = 2.0 \text{ A}$

(b) $P_o = \frac{V_o^2}{R}$
 $P_o = \frac{(\sqrt{2}V_s)^2}{R}$
 $P_o = \frac{(\sqrt{2} \times 240)^2}{120}$
 $P_o = 960 \text{ W}$

